


Code No: R5310404

III B.Tech I Semester(R05) Supplementary Examinations, December 2009  
 DIGITAL IC APPLICATIONS  
 (Common to Electronics & Communication Engineering and Electronics & Instrumentation  
 Engineering)

Time: 3 hours

Max Marks: 80

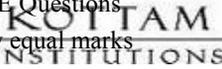Answer any FIVE Questions  
 All Questions carry equal marks



1. (a) Design a CMOS transistor circuit that realizes the following Boolean function.

$$f(x) = (a + b). (b + c)$$

Also explain its functional operation.

- (b) What are the parameters that are necessary to define the electrical characteristics of CMOS circuits? Mention the typical values of a CMOS NAND gate. [8+8]
2. (a) Design a three input NAND gate using diode logic and a transistor inverter? Analyze the circuit with the help of transfer characteristics.
- (b) Explain sinking current and sourcing current of TTL output? Which of the parameters decide the fan-out and how? [8+8]
3. (a) Write a VHDL Entity and Architecture for the following function?

$$F(x) = a \cdot b \cdot c$$

Also draw its relevant logic diagram.

- (b) Explain the use of Packages Give the syntax and structure of a package in VHDL. [8+8]
4. Design the logic circuit and write a data-flow style VHDL program for the following functions?
- (a)  $F(A) = \sum p,q,r,s (1, 3, 4, 5, 6, 7, 9, 12, 13, 14)$
- (b)  $F(X) = \sum SA,B,C,D (3, 5, 6, 7, 13) + d (1, 2, 4, 12, 15)$  [8+8]
5. Design a two-digit BCD adder with logic gates. Using this logic write the VHDL program in structural style of modeling. [8+8]
6. (a) Design a 16-bit comparator using 74X85 ICs.
- (b) Write a behavioral VHDL program to compare 16-bit signed and unsigned integers. [16]
7. (a) Design a 3-bit LFSR counter using 74X194 List out the sequence assuming that the initial state is 001.
- (b) Explain with timing waveforms, different operations during one clock cycle in a synchronous system structure. [8+8]
8. (a) Determine the ROM size needed to realize the logic function performed by 74X153 and 74X139.
- (b) Design an 8×8 diode ROM using 74X138 for the following data starting from the first location. [8+8]

*AB, 52, 74, 0F, CA, 9D, 2F, E6*